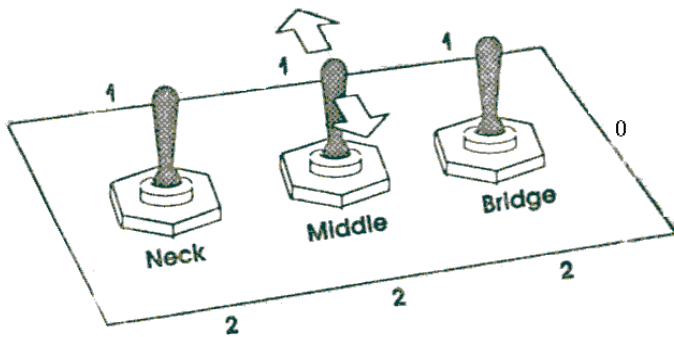


# Dan Armstrong's Super Strat



Get 12 pickup combinations with this replacement selector setup. Drill 3 holes in the slot of the normal strat selector switch and put these three mini-toggle switches in its place.

Parts: 2 on-on mini-toggles  
1 on-on-on mini-toggle  
a fair amount of wire

from Guitar Player Magazine 1987

N - M - B			
2	1	0	Neck only
1	2	0	Middle only
1	1	2	Bridge only
2	2	0	Neck and Middle Parallel
2	1	2	Neck and Bridge Parallel
1	2	2	Middle and Bridge Parallel

N - M - B			
2	2	2	All Parallel
1	1	0	Neck and Middle Series
2	1	1	Neck and Bridge Series
1	2	1	Middle and Bridge Series
1	1	1	All Series
2	2	1	Neck and Middle Parallel w/ Bridge Series